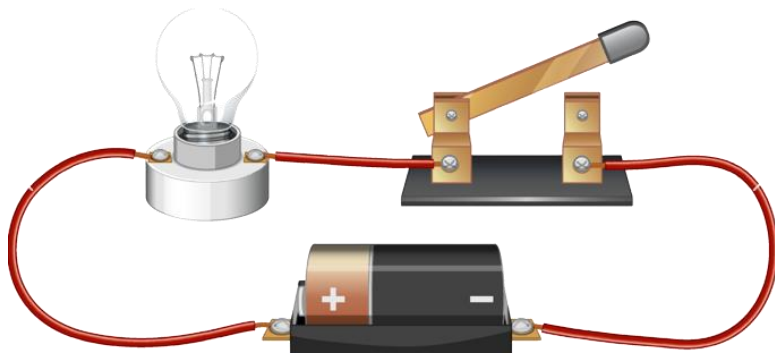


CIRCUITS

Electrical energy flows along paths known as _____.

Circuits are _____ when there is no break and energy can flow continuously. Circuits are _____ when there is a break and energy cannot flow continuously.



Series Circuits

- A series circuit allows electrical charges to flow along only one SINGLE path

Parallel Circuits

- A parallel circuit allows electrical charges to flow through more than ONE path